



References


(only some very basic things)

P. Fischer, Heidelberg University



Goal

 - To bias chips, we need a **reference** voltage or current
- This should be ‘constant’, i.e. mostly independent of
 - Process variations (Thresholds, resistor values,...)
 - Supply Voltage
 - Temperature
- Jargon: ‘PVT independent’. Output of a circuit:




- To asses quality of a reference circuit, study
 - Power Supply Rejection Ratio (PSRR): relative change of V_{REF} vs relative change of V_{Supply}
 - Temperature Rejection (rel. change of V_{REF} per degree K)



Implementation

 - Very common implementation principle:
 - Look for two different $I(U)$ dependencies and find the intersection



- There are normally 2 intersections!
 - Need **startup circuit** to avoid wrong operation point





Getting Rid of Temperature Dependence

- Most component properties depend on temperature
- To obtain temperature independence, add two quantities with opposite temperature dependency
- Jargon:
 - PTAT = Proportional To Absolute Temperature
 - NTAT = Negative To ..



Using a Diode (or BJT)

- Diode current $I_D \sim I_S(T) \text{ Exp}(V_D/U_{th}) \rightarrow V_D = U_{th} \ln(I_D/I_S(T))$
 - $U_{TH} = kT/q \sim 25\text{mV} @ RT$ (PTAT!)
 - I_S depends on diode geometry etc.
 I_S also depends on temperature!
- The temperature dependency of $I_S(T)$ is quite strong so that ***overall***, the diode voltage (at constant current) ***drops*** with increasing temperature, i.e. it is **NTAT**:

  




Typical Reference Topology

- Consider circuit shown right.

Assume $V_1 == V_2$

 

- $V_R + U_{th} \ln(I_D/kI_S) = V_1 == V_2 = U_{th} \ln(I_D/I_S)$
- $\rightarrow V_R = U_{th} \ln(I_D/I_S) - U_{th} \ln(I_D/kI_S)$
 $= U_{th} [\ln(I_D/I_S) + \ln(kI_S/I_D)]$
- $\rightarrow V_R = U_{th} \ln(k)$ (!) (if I_D is equal on both sides)
 - independent of diode parameters !
 - independent of supply voltage !
- BUT: U_{th} still depends on temperature... (PTAT)






Diode / BJT

- Often a (parasitic) Bipolar Junction Transistor (BJT) is used because
 - It has a better model
 - It contains no parasitic elements
 - Forward biased diodes are normally not allowed




How to Achieve $V_1 == V_2$?

   - 1 Use identical cascode MOS with
 - same gate voltages
 - identical currents (i.e. we must make sure $I_1 == I_2$)
- 2 Use a mirror to assure $I_1 == I_2$
- 3 Use a Diode connection to find V_{casc}
Why on the right side? (Hint: $V_1 == V_2$ should not be fixed!)





Sample Implementation of a Reference

 

- Temperature **independence** is obtained if the temp-slopes of PTAT and NTAT just **cancel out**
- PTAT contribution can be tuned by adjusting e.g. R_2
- Requires good models to find right choice! Make test chips!



‘Curvature Correction’


- The Diode voltage is no perfectly linear NTAT
- The ‘quadratic’ term is not cancelled out with such a simple circuit (% effect)
- More advanced circuits try to correct the remaining ‘curvature’



Another Very Simple Reference

- This version ‘uses the Cascode MOS as diodes’

MOS in weak inversion:

 

$$I_D = I_{DO} e^{\frac{V_G}{nU_{Th}}} e^{\frac{-V_S}{U_{Th}}}$$

$$I_0 = m I_{DO} e^{\frac{V_1}{nU_{Th}}} e^{\frac{-V_2}{U_{Th}}}$$

$$I_0 = I_{DO} e^{\frac{V_1}{nU_{Th}}}$$


$$I_0 = V_2 / R$$

$$\Rightarrow I_0 = \frac{kT}{q} \frac{\ln m}{R}$$



Independent of technology parameters (but PTAT)!

Layout:
300µm x
100µm

 



Why Weak Inversion ?

Weak Inversion:



$$I_D = I_{DO} e^{\frac{V_G}{nU_{Th}}} e^{\frac{-V_S}{U_{Th}}}$$

$$I_0 = m I_{DO} e^{\frac{V_1}{nU_{Th}}} e^{\frac{-V_2}{U_{Th}}}$$

$$I_0 = I_{DO} e^{\frac{V_1}{nU_{Th}}}$$

$$I_0 = V_2 / R$$

$$\Rightarrow V_2 = \frac{kT}{q} \ln m$$

  

Strong Inversion:

$$I_D = \frac{K}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$I_0 = m \frac{K}{2} \frac{W}{L} (V_1 - V_2 - V_T)^2$$

$$I_0 = \frac{K}{2} \frac{W}{L} (V_1 - V_T)^2$$

$$I_0 = V_2 / R$$

$$\Rightarrow V_2 = \frac{\sqrt{m}-1}{m} \frac{1}{\frac{W K}{L^2} R}$$


Depends from Process Parameters





Minimal implementation

- Make currents equal with PMOS mirror:

 


- Early effects in MOS lead to poor mirror ratios at changing supply voltage -> poor PSRR
 - Can add Cascodes!





Detailed Schematic with Cascodes

 - NMOS operate in weak inversion
- Resistor is P+ poly
- All MOS are cascaded using low voltage cascode circuits
- A reset signal forces node 'res' to ground
-> current flows in circuit for guaranteed start





Measurements

  

- Very high output resistance of $R_{\text{out}} > 200 \text{ M}\Omega$
- Reference works at 1 V !