



Exercise: CAM - Part 1

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg




Background

- For an understanding on SRAMs and CAMs, see the lecture slides on the course web page.



SRAM_Cell

 - Create schematic and symbol of a SRAM_cell




- Pins should be: **Bit**, **BitB**, **Word**
- Use global nets vdd! and gnd! for the supplies
- Use minimal lengths for the NMOS
- Use WNWRITE for the write NMOSs, start with 0.44um
- Use WNINV for the other NMOS, start with 0.44um
- Use WPINV = minimum and LPINV = minimum for the PMOS



Simulating ONE SRAM cell

 - Create the following schematic SRAM_SIM



- Use wide (10 μm), minimum length MOS for driving
- You can use a VCVS for the inverter (how ? ...)
- Create control signals which
 - Write 0 to the SRAM, then read it back. Then try writing 1.
 - You can create a signal with multiple pulses by stacking vpulses
 - Use for instance 5ns for precharge



Simulating MULTIPLE cell

- Add a second SRAM cell on the same bitlines ('below')
 - You also need a further control signal Word2

- Create signals for the following sequence
 - Write 0 to the first RAM cell
 - Write 1 to the second RAM cell
 - Read back the first cell
 - Read back the second cell

 - Make a drawing of the signals on paper first!
 - Work e.g. in steps of 5 ns

- Add additional capacitance to the bit lines until the circuit stops working




Transistor Dimensions

- Play with the dimensions of the transistors
- Find out in which ranges the cell works
- Check robustness:
Add an OFFSET of, say, 0.1V to one of the inverters in the SRAM cell (using a VDC source) and repeat the above exercise.



CAM Cell

 - Starting from the SRAM cell, make a CAM cell



- Add a **match** signal
- Use minimal length NMOS with **WNMATCH**
- Simulate the cell in schematic **CAM_SIM**:
 - Write 0 as before
 - Precharge the match line
 - Present comparison data at the bit lines (once matching, once mismatching)



Layout – With substrate and NWEELL contacts

- In the layout
 - Word and Match shall run horizontally
 - the two bit lines vertically
 - Power can go either way
 - Use only M1 - M3
 - Start with substrate and NWEELL contacts *in* the CAM cell
- Before going in layout details, investigate on a paper various options for component and bus placement
 - Make sure cells can be placed directly adjacent to each other (maybe flipped or mirrored)
 - Try to minimize the NWEELL area (and spacings) required
 - Keep your findings on 'good' (or 'bad') transistor sizes in mind!



Layout – More compact

The contacts in each cell take quite some space and are not really needed. It is sufficient to contact substrate and NWEELL 'here and there'.

If you want:

- Do *not* put substrate or NWEELL contacts in each CAM cell.
- Make sure the wells of adjacent cells overlap
- Try to get the cell DRC and LVS clean.
 - You may need to add two more pins...
- Make a row of 8 horizontally abutted cells, and add one substrate and well contact. Make sure you can abut these groups.
- Make a schematic (using bus notation!) and LVS.