



# Exercise: CAM – Part 2: RAM Sense Amplifier

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation  
Uni Heidelberg




# Decision Speed

- We deal here with 'normal' reading of the SRAM cells (not with CAM decision making)
- So far, the NMOSs in the SRAM cell must discharge the Bit/BitB busses down to the threshold of the following logic, i.e. by roughly  $V_{DD}/2$ .
- When many rows are connected, the Bit/BitB capacitance becomes large and the discharge is slow.


 
# Simplified Simulation

- To simulate, we simplify the situation to the minimum:
  - A 'SRAM cell' set to a fixed value
  - We add an additional bus capacitance of, say,  $C_{BUS} = 5\text{pF}$




- Simulate how long it takes to discharge Bit to  $VDD/2$ .
- Is this consistent with a calculation ?
  - You need to determine the current in M1 by simulation


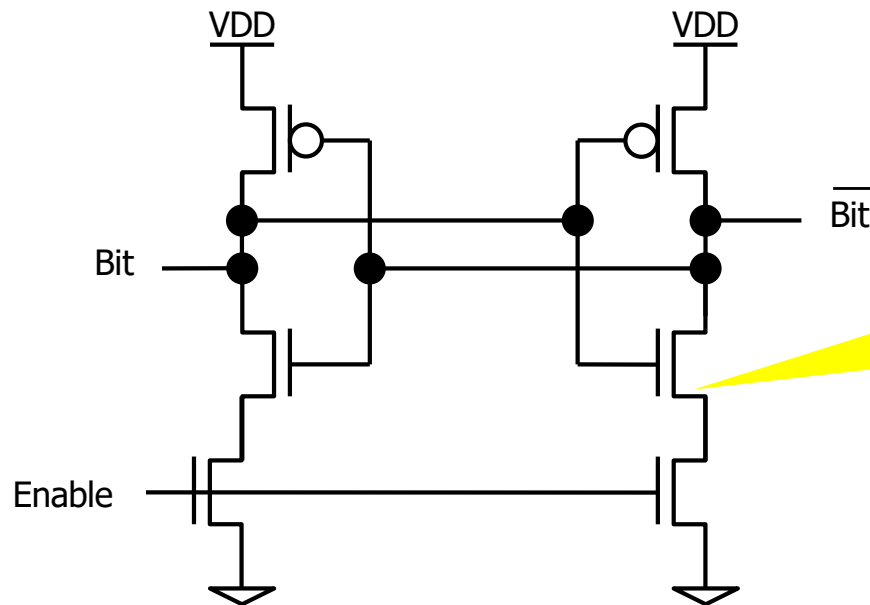
# A Sense Amplifier

- Add a 'sense amplifier' which consists of a cross coupled inverter pair which can be turned on/off:
  - When enable = 0, the circuit is inactive
  - When enable = 1, *one side* is pulled low (the other is *pulled up*)



- The 'side' which is pulled low is determined by *an initial mismatch*, introduced via Bit and BitN.
- Activate the circuit shortly after you enabled the wordline
  - How much faster is the discharge on Bit?




# Getting Rid of the Bus Capacitance

- Our sense amplifier (SA) still has to discharge the full bus capacitances.
  
- Add a switch between the **Bit/BitB** busses and the SA and open it just when the SA is enabled.
  - Do you need a NMOS or a PMOS?
  - How does the discharge speed at the SA side change?
  
- Try to **NOT** open the switch.
  - What happens? How do you explain that?
  
- **Comment:**
  - It is more important to have **Bit** and **BitB** be equal before evaluation than to have them at VDD. Therefore a switch shorting **Bit** and **BitB** is often used.


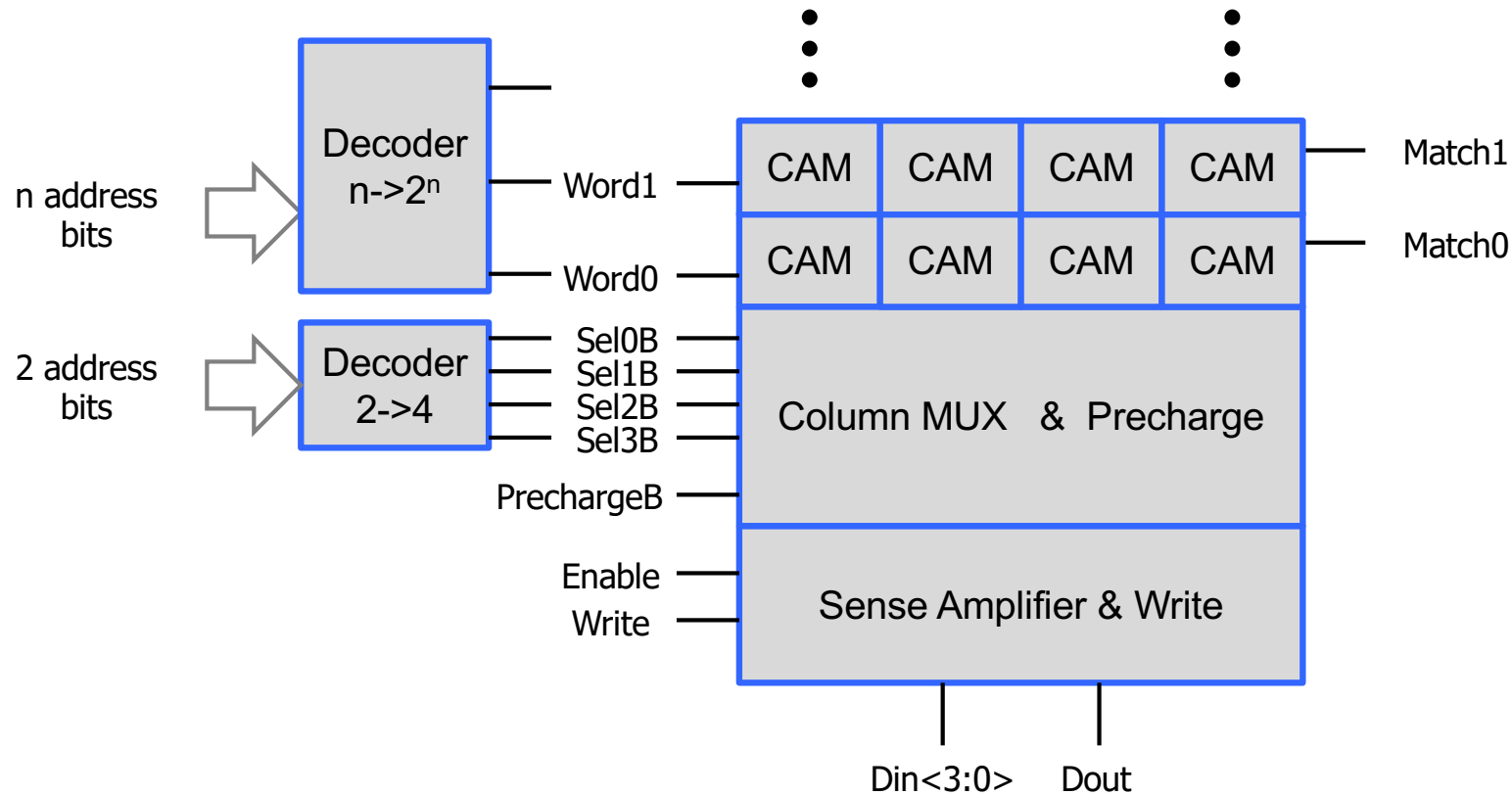
# Column Multiplexors

- The SA is normally too large (it uses larger MOS) to fit in *one* SRAM / CAM column
- Therefore, several columns are *multiplexed* onto one SA
- A typical arrangement looks like this:





# Putting Everything Together

- Make a schematic which has the above structure
  - Merge precharge and column-MUX
  - Think about how to merge the sense amplifier and the Write mechanism. There are many possibilities.  
You could keep the write part parallel for all 4 bits
  
- Simulate everything
  - We will soon see how to use a 'mixed mode simulation' to better generate the many control signals....
  
- Make a layout of the MUX and SA which matches your CAM cell and combine the 3 parts