



Exercise: CAM - Part 3

Prof. Dr. P. Fischer

Lehrstuhl für Schaltungstechnik und Simulation
Uni Heidelberg



Larger CAM

- Create a larger CAM Block with at least 2 x 2 cells
 - Connect to word and match lines and the bit lines
 - Use advanced syntax (busses) to make it nicely compact
 - Best introduce a 'CAM Row' or 'CAM Column' cell.

- Set up a mixed mode simulation
 - Write different words
 - Present comparison words and check the match.
Create a case with a 'hit' and a case without a hit
 - Feed back the match lines to your Digital module and make a comparison of the result in your HDL code